



4. Find the following:

Find  $I_T$ ,  $R_T$  and  $V_A$  via *analysis* (show all work.)

$R_{123} = 1128.456$

$R_{45} = 2000$

$R_{67} = 9400$

$R_{4567} = 1649.123$



$R_T = 2777.579$

$I_T = 0.00324$

$I_1 = 2.67E-03$

$I_2 = 5.68E-04$

$V_A = 5.34$

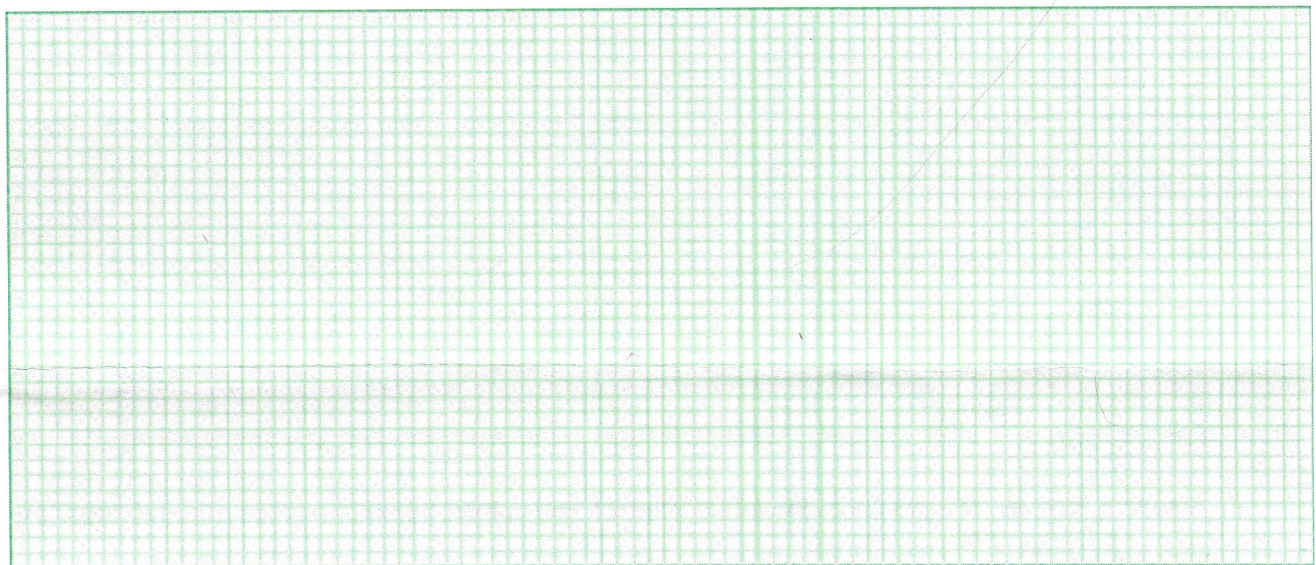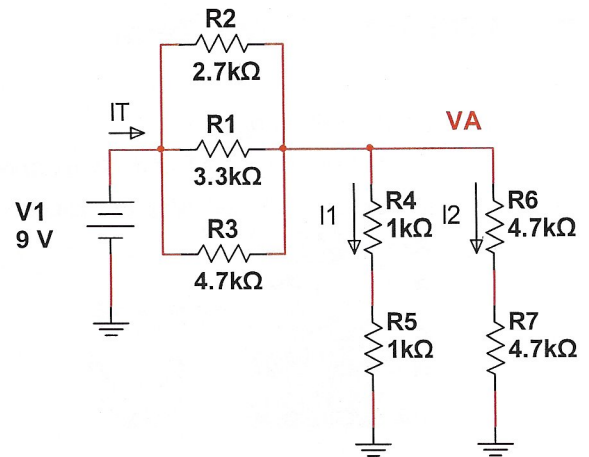

Find  $I_1$ ,  $I_2$ ,  $I_T$ ,  $R_T$  and  $V_A$  via *simulation* (capture and upload simulation schematic and outputs)

$R_{123} = 1.134k$

$R_{45} = 2003$

$R_{67} = 9400$

$R_{4567} = 1649$

$R_T = 2777$

$I_T = 3.24mA$

$V_A = 5.34$

Find  $I_T$ ,  $R_T$  and  $V_A$  via *test* (capture your test setup and measure all resistors,  $V_A$ ,  $I_1$ ,  $I_2$ , and  $I_T$ ).

$R_1 = 3.297$     $R_2 = 2.6882$     $R_3 = 4.6217$     $R_4 = 1.0026$     $R_5 = 1.9990$

$R_6 = 4.691$     $R_7 = 4.644$     $R_T = 2762.59$

$I_1 = 2.68mA$     $I_2 = 5.75mA$     $I_T = 3.258mA$     $V_A = 5.35$

2. Find the following:

Find  $I_T$ ,  $R_T$  and  $V_A$  via *analysis*

(show all work, can also use Excel)



$R_{12} = \underline{5000}$

$R_{34} = \underline{2000}$

$R_T = \underline{7000}$

$I_T = \underline{1.29 \text{ E-}03}$

$V_A = \underline{2.57 \text{ V}}$

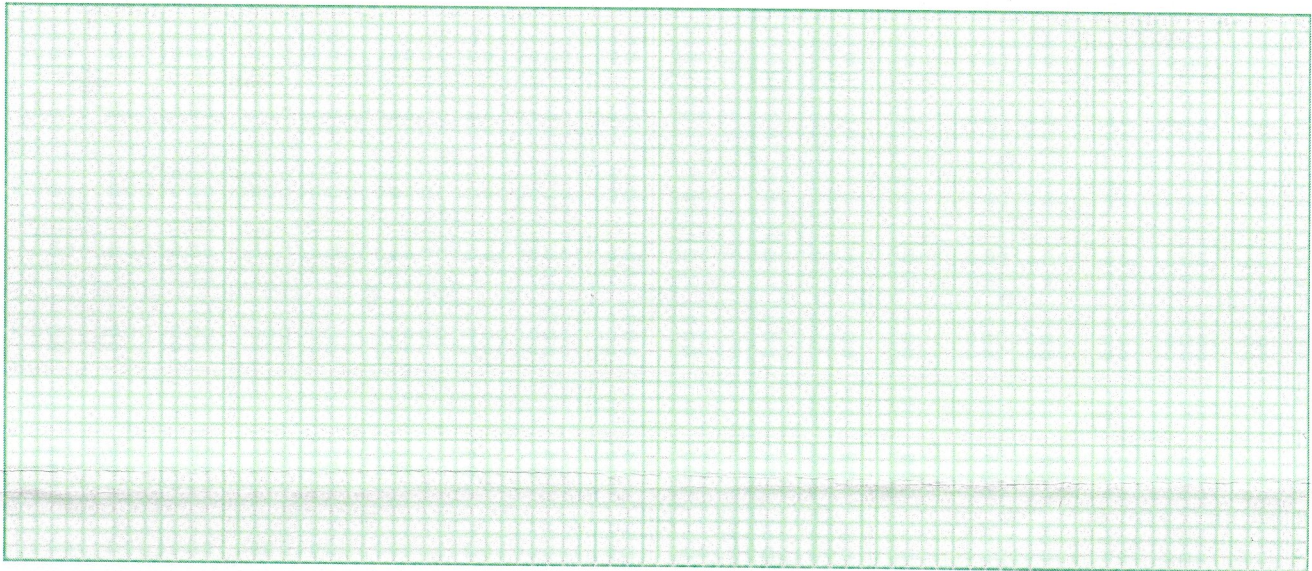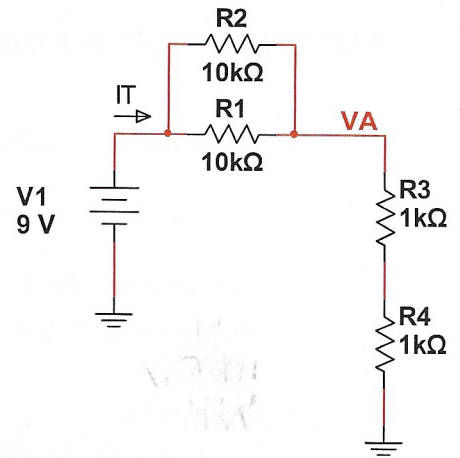

Find  $R_{12}$ ,  $R_{34}$ ,  $R_T$ ,  $I_T$  and  $V_A$  via *simulation* (capture and upload simulation schematic and outputs)

$R_{12} = \underline{5000}$

$R_{34} = \underline{2000}$

$R_T = \underline{7016}$

$I_T = \underline{1.29 \text{ mA}}$

$V_A = \underline{2.57}$

Find  $I_T$ ,  $R_T$  and  $V_A$  via *test* (capture your test setup and measure all resistors,  $V_A$  and  $I_T$ ).

$R_1 = \underline{10.097 \text{ k}}$

$R_2 = \underline{9.952 \text{ k}}$

$R_3 = \underline{1.9283 \text{ k}}$

$R_4 = \underline{1.0015 \text{ k}}$

$R_T = \underline{6.999 \text{ k}}$

$I_T = \underline{1.2832 \text{ A}}$

$V_A = \underline{2.5704}$