

Name Brandon Steup Date \_\_\_\_\_

Lab Partner's Name Covey King

Score \_\_\_\_\_ Instructor (Mr. Bell)

Lab Partner's Name Tung Doan

The following questions should be should be answered in three ways: either using your calculator or Excel, simulation using MultiSim and test using Elvis II. You can use back of test to show work!



1. Find the following:

Find  $I_T$ ,  $R_T$  and  $V_A$  via *analysis* (show all work, can also use Excel)

$R_T = \underline{9.400 \text{ k}\Omega}$

$I_T = \underline{957.4 \text{ }\mu\text{A}}$

$V_A = \underline{4.5 \text{ V}}$

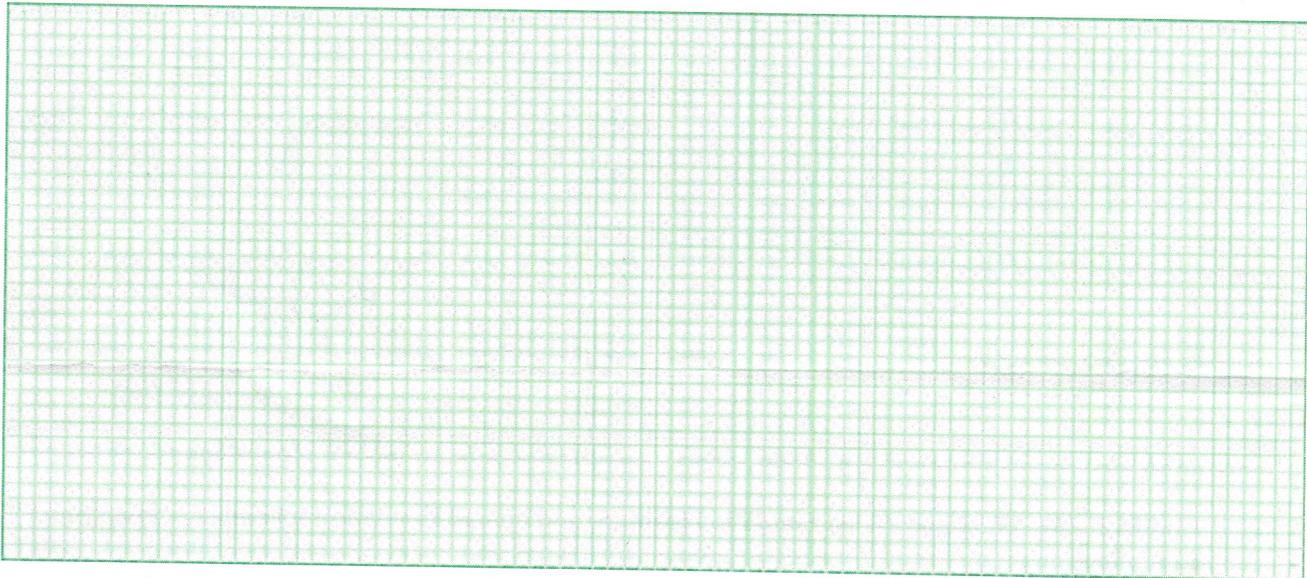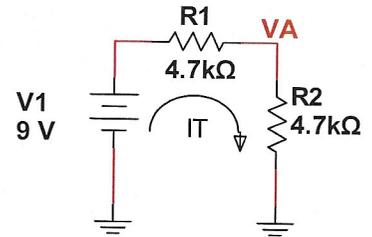

Find  $I_T$ ,  $R_T$  and  $V_A$  via *simulation* (capture and upload simulation schematic and outputs)

$R_T = \underline{9.413 \text{ k}\Omega}$

$I_T = \underline{957 \text{ }\mu\text{A}}$

$V_A = \underline{4.5 \text{ V}}$

Find  $I_T$ ,  $R_T$  and  $V_A$  via *test* (capture your test setup and measure all resistors,  $V_A$  and  $I_T$ ).

$R1 = \underline{4.624 \text{ k}\Omega}$

$R2 = \underline{4.656 \text{ k}\Omega}$

$R_T = \underline{9.282 \text{ k}\Omega}$

$I_T = \underline{0.9720 \text{ mA}}$

$V_A = \underline{9.533 \text{ V}}$

11/145

3. Find the following:

Find  $I_T$ ,  $R_{12}$ ,  $R_{34}$ ,  $R_T$  and  $V_A$  via *analysis*

(show all work, can also use Excel)



$R_{12} = 3197.279$

$R_{34} = 3200$

$R_T = 6397.279$

$I_T = 1.41 \text{ mA}$

$V_A = 4.50 \text{ V}$

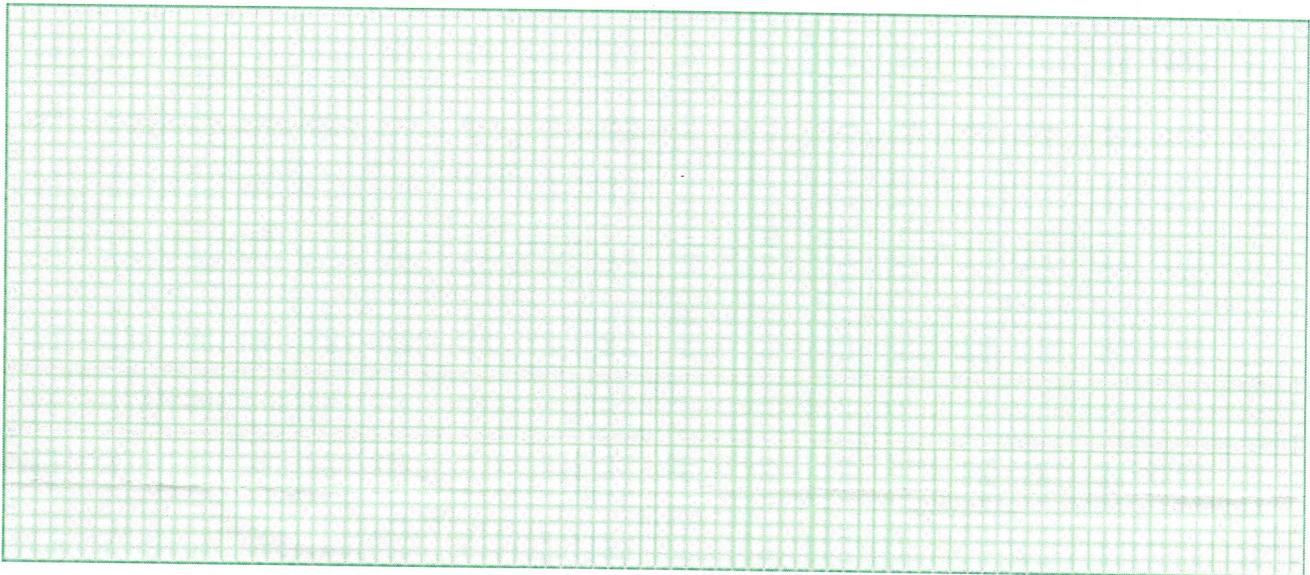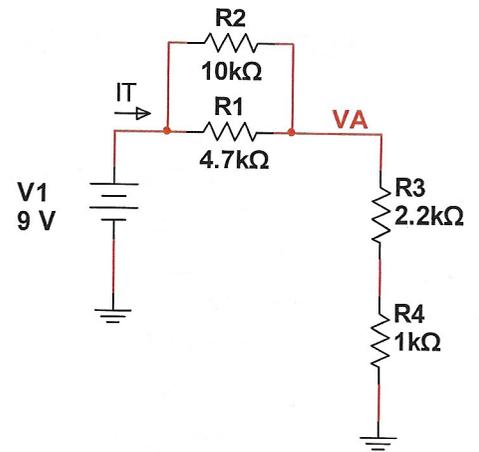

Find  $R_{12}$ ,  $R_{34}$ ,  $R_T$ ,  $I_T$  and  $V_A$  via *simulation* (capture and upload simulation schematic and outputs)

$R_{12} = 3197.279$

$R_{34} = 3200$

$R_T = 6.411 \text{ K}$

$I_T = 1.41 \text{ mA}$

$V_A = 4.50$

Find  $I_T$ ,  $R_T$  and  $V_A$  via *test* (capture your test setup and measure all resistors,  $V_A$  and  $I_T$ ).

$R_T = 6.373 \text{ K}$

$R_1 = 4.623 \text{ K}$

$R_2 = 10.090 \text{ K}$

$R_3 = 2.1997 \text{ K}$


$R_4 = 1.607 \text{ K}$

$I_T = 1.4075 \text{ A}$

$V_A = 4.578 \text{ V}$

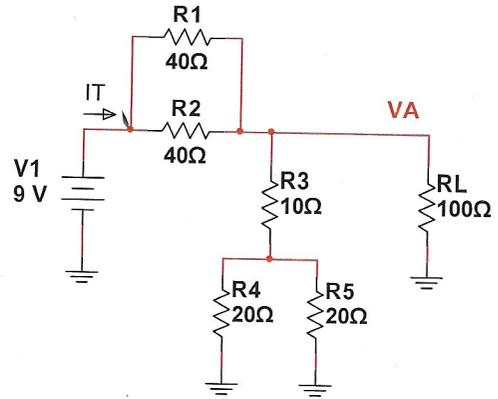5. Find the following :

Find  $R_{TH}$ ,  $V_{TH}$  and  $R_L$  for maximum power transfer via analysis (show all work.) Create a plot in Excel for the power transfer.



$R_{TH} = 4$   
 $V_{TH} = 1.5V$   
 $R_L = 100$

$V_1 \cdot 20 /$

$9 \cdot 20 / 20 + 10 + 10$



Find  $R_{TH}$ ,  $V_{TH}$  and  $R_L$  for maximum power transfer via simulation (capture and upload simulation schematic and outputs).

$R_{TH} = \underline{\hspace{2cm}}$

$V_{TH} = \underline{\hspace{2cm}}$

$R_L = \underline{\hspace{2cm}}$