


## Class Sessions

Week 2. Chapter (2)

Juddo Abaker

Analysis Questions.

6/ Drawing a schematic.

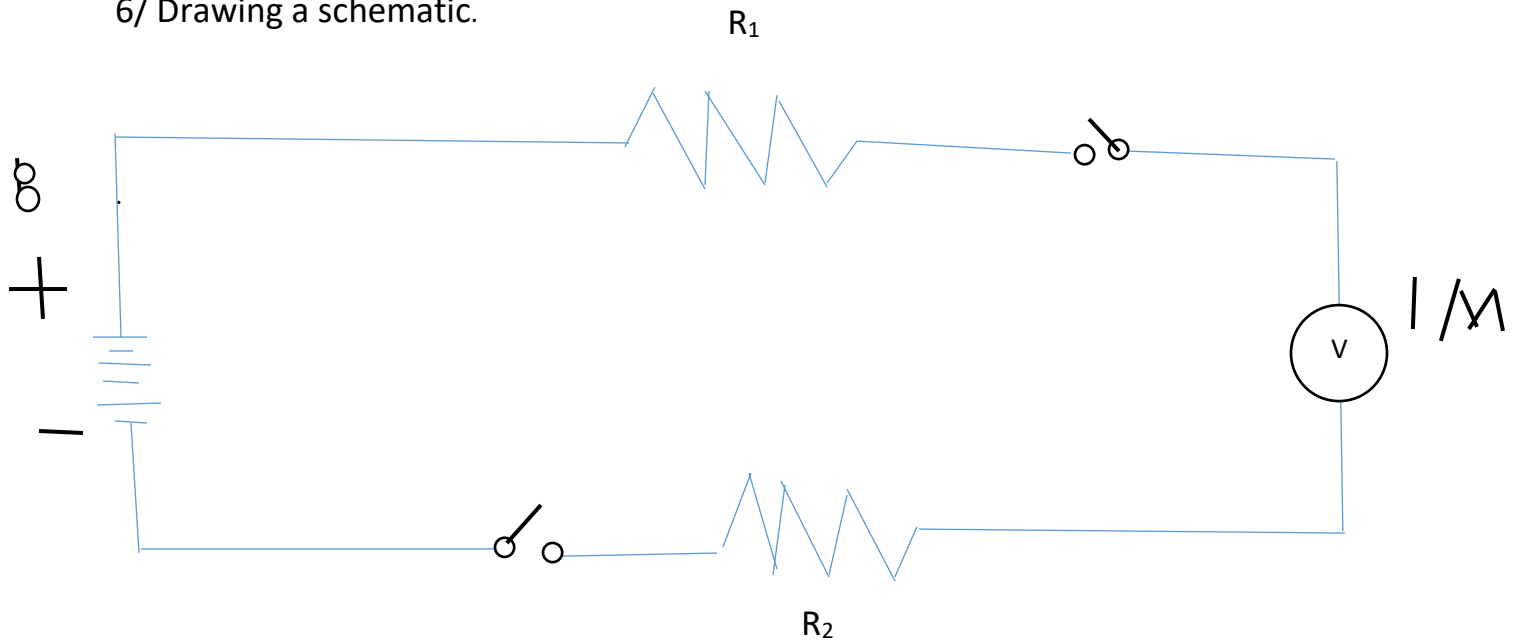


7/ List of color coding resistors.

- Brown, black, red and silver.
- Red, violet and orange.
- Brown, black, green and silver.
- Brown, black, black and gold.

Juddo Abaker

EECT-111-S1C-C1 Chapter (3).

HW. Problems.

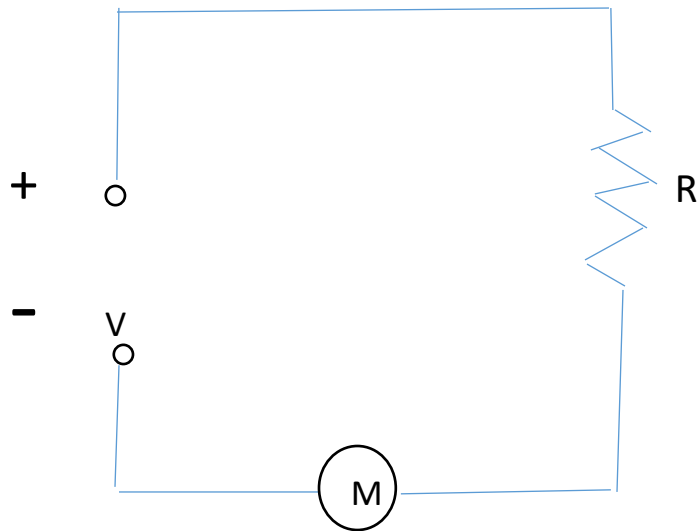

FIGER 3-7

7.  $V=IR$  then  $R=V/I$  so  $R=41V/50Ma=.82\Omega=820\Omega$

10.  $180w*1/3 = 60W$

13. Power will increase,  $P=V*I$ .so, I is same and V doubled.

21.  $V=\text{sqr- of } PR$ . Then  $V=\text{sqr of } 100Mw*10K\Omega = 31.6227766^2=1000mv= 100V$

$R_1 = 12k\Omega$

Juddo Abaker

EETC-111

HW-Chapter (4)

20.  $R_T = R_1 + R_2 + R_3 + R_4 + R_5 + R_6$

$$R_T = 1K\Omega + 47K\Omega + 10K\Omega + 27K\Omega + 5K\Omega + 1K = 91K\Omega$$

$$V_T = I_T \times R_T$$

$$R_4 = 27K\Omega$$

$$V_4 = 54K\Omega$$

$$I_4 = V_4 / R_4 = 54V / 27K\Omega = 2mA$$

$$V_T = (2mA \times 91\Omega) = 182V$$

- a.  $V_2 = I_2 \times R_2 = (2mA \times 47K\Omega) = 94V$
- b.  $V_3 = I_3 \times R_3 = (2mA \times 1k\Omega) = 2V$
- c.  $I_T = 2mA$
- d.  $P_T = V_T \times I_T = (182V \times 2mA) = 364mW$

New.

$$R_T = 91K\Omega$$

$$P_T = 2(364mW) = 728mW$$

$$P_T = V_T^2 / R_T$$

$$V_T = \text{square root of } (728mW)(91K\Omega) = 257.39V$$

$$I_T = \text{square root of } P_T / R_T = \text{sqrt of } 728mW / 91k\Omega = 2.83mA$$

26. the circuit applied voltage increase.

Chapter (5).

$$8. V_T = I_T \times R_T$$

$$R_T = 40V / 10mA = 4k\Omega$$

$$1/R_T = 1/6k\Omega + 1/R_1$$

$$1/4k\Omega = 1/6k\Omega + 1/R_1$$

$$1/R_1 = 1/4k\Omega - 1/6k\Omega$$

$$1/R_1 = 1/12k\Omega$$

$$9. v_2 = (2A)(25\Omega) = 50V$$

$$V_1 = V_2 = 50V$$

$$I_1 = 2.5A - 2 = 0.5A$$

$$P_1 = V_1 I_1 = (50V)(0.5A) = 25W$$

$$13. 1/R_T = 1/R_x + 1/R_1 + 1/R_2 + 1/R_3 + 1/R_4$$

$$1/10K\Omega = 1/R_x + 1/100K\Omega + 1/47K\Omega + 1/27K\Omega$$

$$1/R_x = 1/10K\Omega - 1/100K\Omega - 1/47K\Omega - 1/27K\Omega = 0.039k\Omega$$

$$1/R_x = 1/0.039k\Omega = 31.56k\Omega$$